

## Power Stage Calculations

The battery voltage range is 2.5V to 3.65V per cell, 37.5V to 54.75V total, and the capacitor voltage will charge up to a bit less than that. To avoid extreme duty cycles, the converter should only be capable of 3:1 voltage step up, which still removes 90% of the capacitor's stored energy. The output current is up to 95A

Output current up to 95A with up to 3:1 voltage step up,  $I_{IN} = 95 \times 3 = 285$  per phase

Input voltage of 18V to 54V

Switching frequency of 500kHz, interleaved to make it effectively 1MHz for the capacitors

$$R_{Load} = V_{Out}/I_{Out} = 3.2 \times 15/150 = 0.32 \text{ ohms}$$

$$\text{Duty Cycle} = 1 - V_I/V_O$$

$$D_{Min} = 0$$

$$D_{Max} = 1 - 18/55 = 67.3\%$$

$$\text{Peak } I_{Out} = 95 \times 2 = 190A$$


$$I_{L(avg)} = \frac{0.5 \times I_{OUT}}{1 - D_{MAX}} \quad I_{PEAK} = I_{L(avg)} + \frac{\Delta I_L}{2} \quad L_{(MIN)} = \frac{(V_{IN(MIN)} - V_{(ON)}) \times D_{MAX}}{f_S \times \Delta I_L}$$

$$I_L = 0.5 \times 190 / (1 - 0.673) = 290.5A$$


$$\Delta I_L = 290.5 \times 0.2 = 58.1A$$

$$I_{Peak} = 290.5 + 58.1/2 = 320A$$
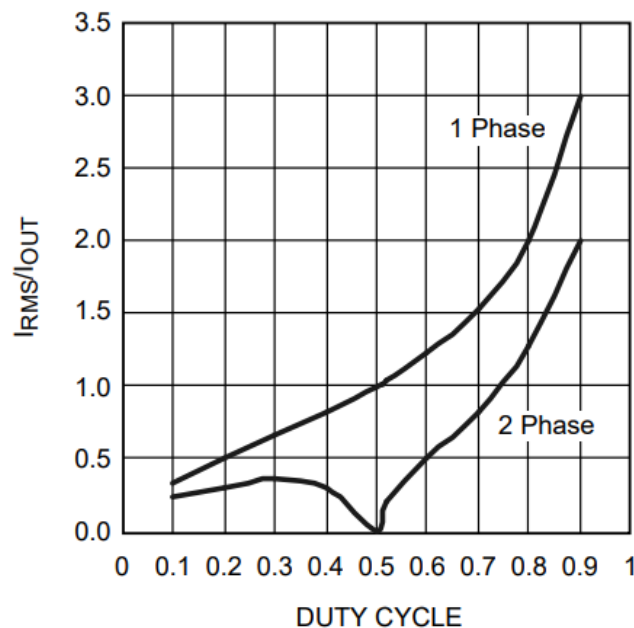
$$L_{Min} = 18 \times 0.673 / (500000 \times 58.1) = 0.417 \text{ uH}$$



$$I_{Cap-RMS} = 0.7 \times 190 = 133A$$

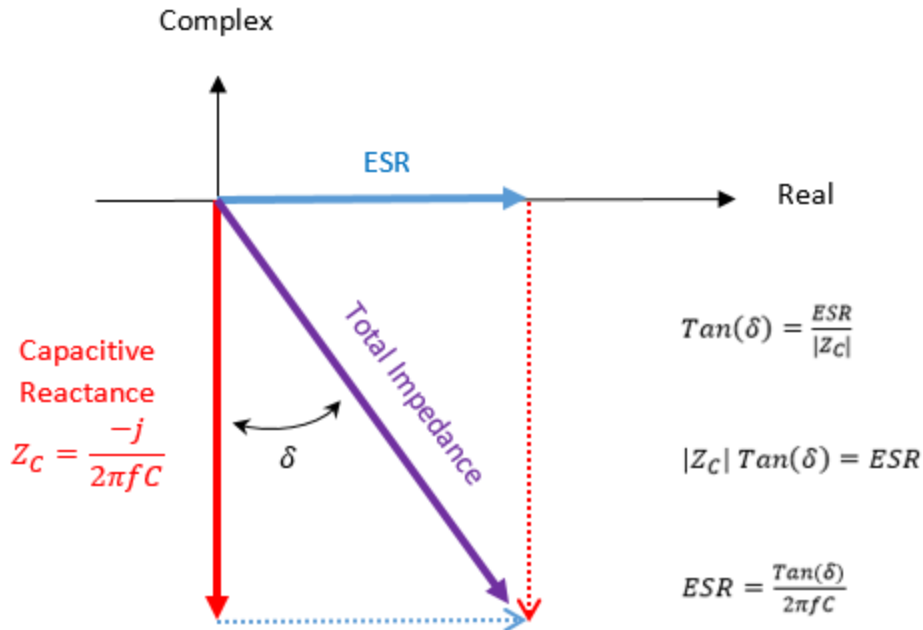


Use 4 x 10uF capacitors, X7R loses 10% of capacitance at 1 MHz, DF = 2.5%

$ESR = DF / (2\pi \cdot f \cdot C) = 0.025 / (2 \cdot 3.14 \cdot 9) = 0.442 \text{ mohms}$

$P_{Cap} = (133/4)^2 \cdot 0.000442 = 0.489 \text{ W}$

$$\Delta V_{OUT} = \frac{I_{OUT(MAX)} \times (1 - D_{MIN})}{f_S \times C_{OUT}} + I_{PEAK} \times ESR$$

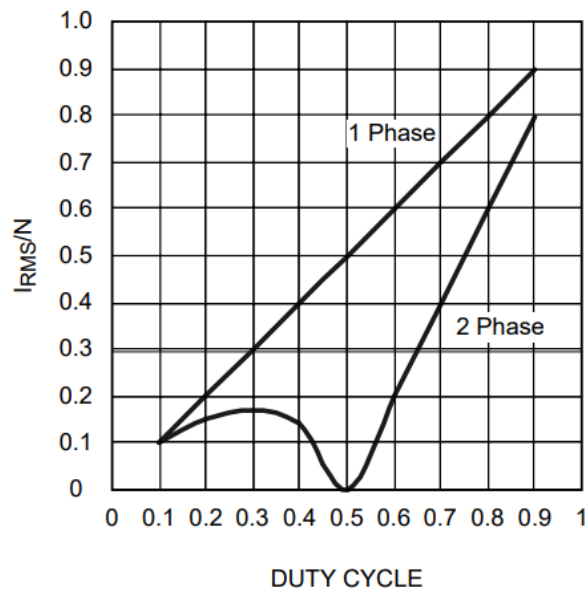$\Delta V_{Out} = 190 \cdot (1 - 0.673) / (10^6 \cdot 4 \cdot 10 \cdot 0.9) + 320 \cdot 0.000442 / 4 = 35.4 \text{ mV}$



$$I_{RIPPLE(Normalized)} = \frac{V_{IN}}{L \times f_S}$$

$I_N = 54 / (0.47 \cdot 0.5) = 230 \text{ A}$

$I_{Ripple} = 0.35 \cdot I_N = 0.35 \cdot 230 = 80.5 \text{ A}$

Again, use 4 x 10uF

$$P_{\text{Cap}} = (80.5/4)^2 \times 0.000442 = 0.179 \text{ W}$$

$$P_{\text{MOSFET}} = \left( \frac{I_{\text{OUT(MAX)}}}{2 \times (1 - D)} \right) \times R_{\text{DS(ON)}} \times D \times 1.3 + V_{\text{IN(MAX)}} \times Q_g \times f_s$$

$$P_{\text{FET}} = 190 / (2 \times (1 - 0.673)) \times 0.0011 \times 0.673 \times 1.3 + 12 \times 0.178 \times 0.5 = 1.35 \text{ W}$$